


## Experiment-7: Keypad 4x4 Matrix

- Interfacing details - Po Pin configuration in the kit for the keypad
  - Scan code look up table for keypad
  - Scanning mechanism
  - Hands On
    - interfacing keypad with 7S display
- Keypad (4 Rows X 4 Columns):
  - The switches SW4 to SW19 are organized as 4 rows X 4 columns matrix.
  - One end of all the switches are connected to port lines P0.4 - P0.7, which is configured as columns.
  - The other end of the matrix is connected to the port lines P0.0 - P0.3 which is configured as rows.
  - The interface diagram for keypad is shown below.

### Operation:

- Initially take one column line to logic HIGH, then check for each row.
- If first row is at logic '0' and other rows are at logic '1' then save the read data and compare with the look-up table.
- Similarly repeat the procedure for all the columns.

Keypad Interface:

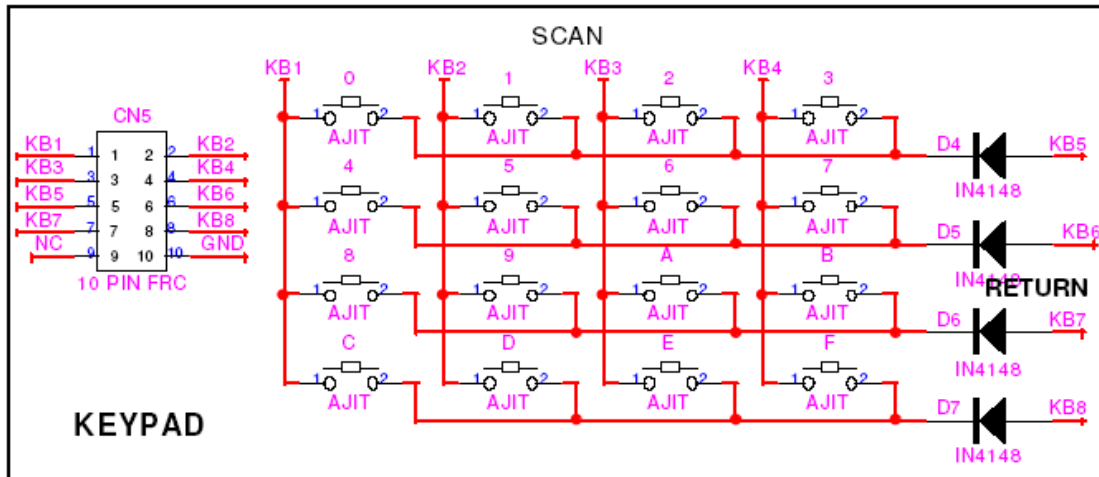

KEY MATRIX

**Key pad Scan Code Table****(Scan column by keeping row low or vice-versa)**

Digit Scan code P0.7 P0.6 P0.5 P0.4 P0.3 P0.2 P0.1 P0.0

0	0xEE	On	On	On	Off	On	On	On	Off
1	0xDE	On	On	Off	On	On	On	on	Off
2	0xBE	On	Off	On	On	On	on	On	Off
3	0x7E	Off	on	on	on	On	On	On	Off
4	0xED	On	On	On	off	On	On	Off	On
5	0xDD	On	On	Off	On	On	On	Off	On
6	0xBD	On	off	On	On	On	On	Off	On
7	0x7D	Off	On	On	On	On	On	Off	On
8	0xEB	On	On	On	Off	On	Off	On	On
9	0xDB	On	On	Off	On	On	Off	On	On
A	0xBB	On	Off	On	On	On	Off	On	On
B	0x7B	Off	on	On	on	On	Off	On	On
C	0xE7	on	on	on	Off	Off	On	on	on
D	0xD7	On	on	Off	on	Off	On	on	on
E	0xB7	on	Off	on	On	off	on	on	on
F	0x77	Off	on	On	on	off	On	on	on

```

//Pseudo code
//Sample Code skeleton for scanning the key press from keypad and displaying it on 7
//Segment displays
//Keypad scan code lookup table
unsigned char scan_code[16]={
    0xEE,0xDE,0xBE,0x7E,
    0xED,0xDD,0xBD,0x7D,
    0xEB,0xDB,0xBB,0x7B,
    0xE7,0xD7,0xB7,0x77
};

//7 Segment code look up table from previous exercise
unsigned char LED_CODE[16]= {
    0x3f,0x66,0x7f,0x39,
    0x06,0x6d,0x6f,0x5e,
    0x5b,0x7d,0x77,0x79,
    0x4f,0x07,0x7c,0x71
};

//main routine
//row by row scanning technique in software
//init all the rows to low and cols to high
//select a 7S display digit to display the key press detected

while(1)
{
    //loop through all the rows
    //assume one row as low
    //scan through the cols to detect the key press
    //send the 7S code for the key press detected
}

```